

① Md. Noyan Ali

Rd1 - 1607021

Objectives of this laboratory are noted below:

i) to know about digital system design mechanism.

ii) to know about adders (half and full), zero/one circuit and arithmetic circuit.


iii) to know how to implement digital circuits using logisim.

iv) to implement arithmetic circuit using logisim and verify outputs.

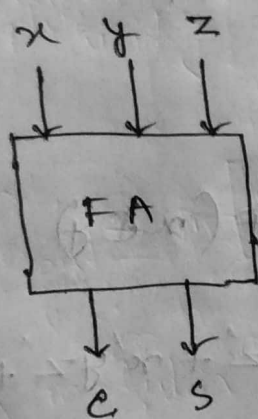v) to implement a circuit using top-down modular fashion.

2

**Introduction:** The most basic arithmetic operation the addition of 2 bits. A combinational circuit that performs this operation is called a half-adder. A combinational circuit that performs the addition of 3 bits is called a full-adder, which can be implemented by 2 half-adders.




x	y	z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder



3

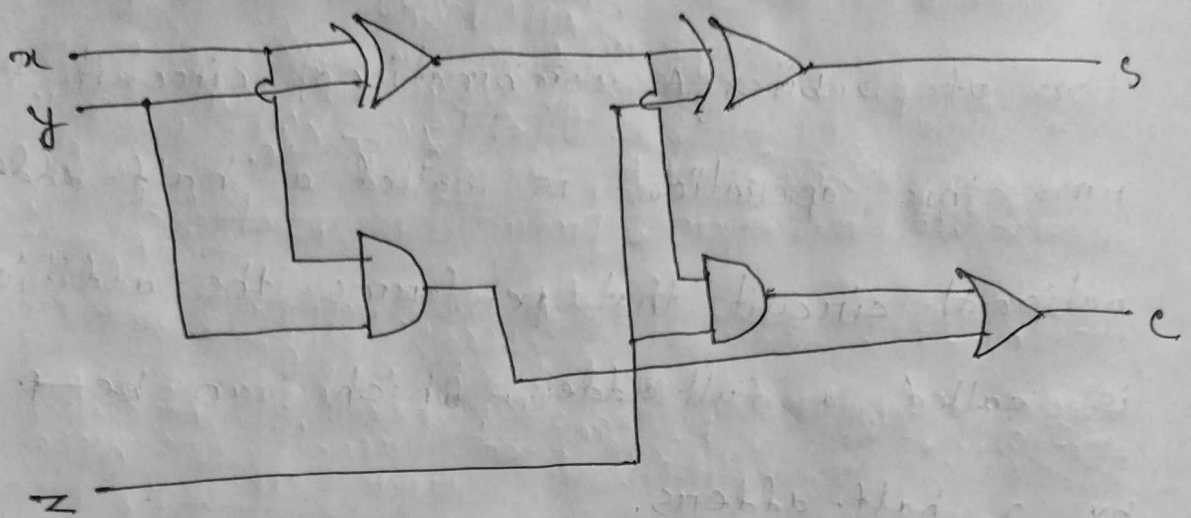

### Implementation of FA

here,

The sum output is,  $s = z \oplus (x \oplus y)$


$$= xy'z' + x'y'z + x'yz + xy'z + x'yz + xy'z + x'yz + xy'z$$

The carry output is,  $c = z(x'y + xy') + xy$

$$= xy'z + x'yz + xy$$

④

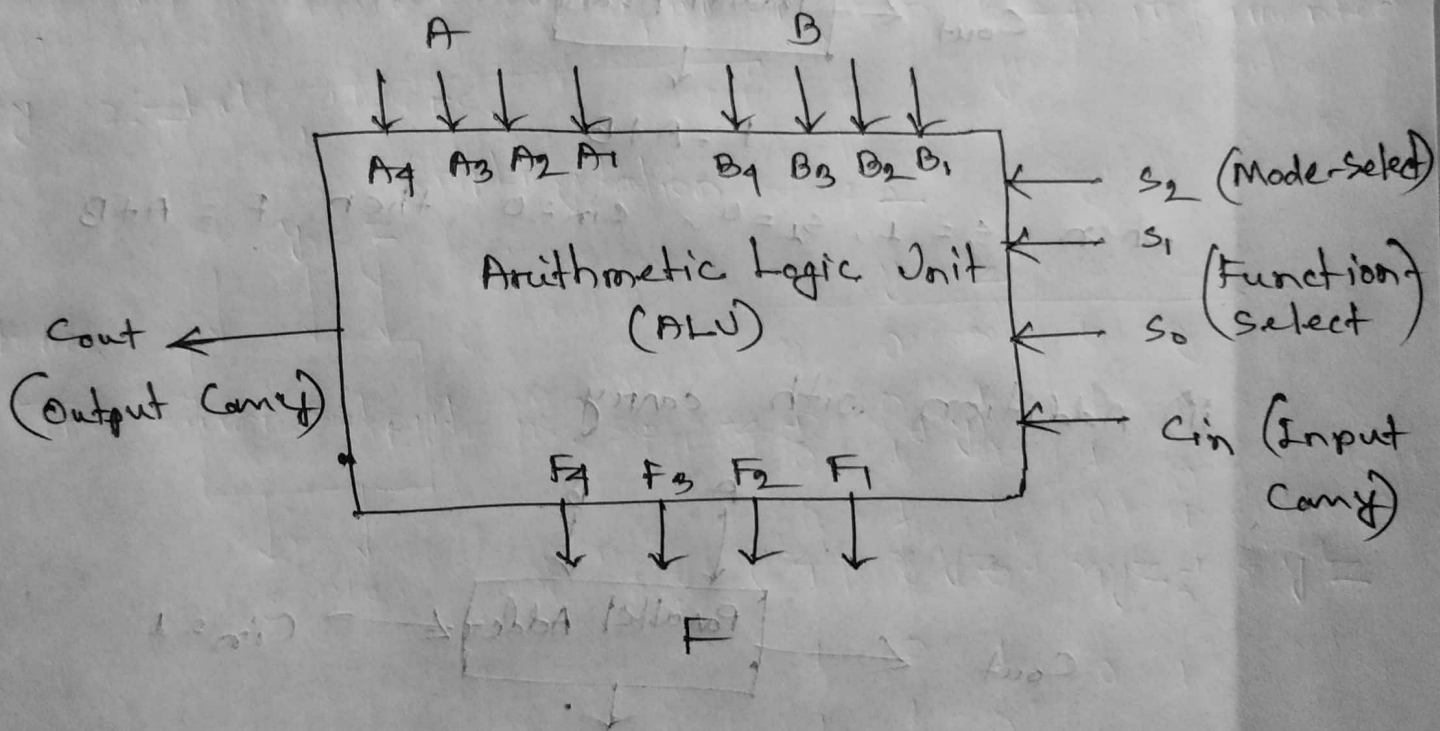**Arithmetic Logic Unit (ALU):** An arithmetic logic unit is a digital circuit used to perform arithmetic and logical operations. It represents the fundamental building block of a computer.




Block Diagram of a 4-bit ALU



5


There are 8 operations of ALU. They are given below:

i) Addition

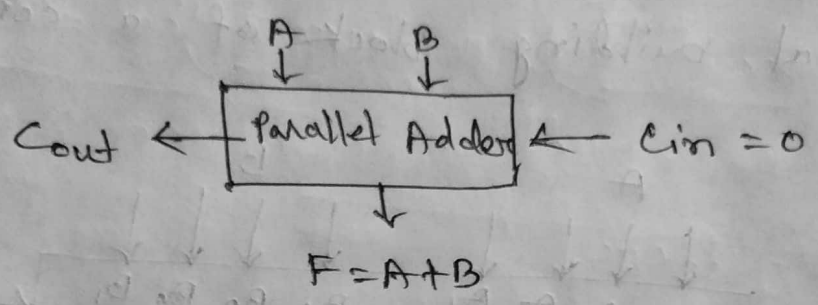

when  $s_0 = 1, s_1 = 0, cin = 0$  then  $F = A + B$


ii) Addition with carry

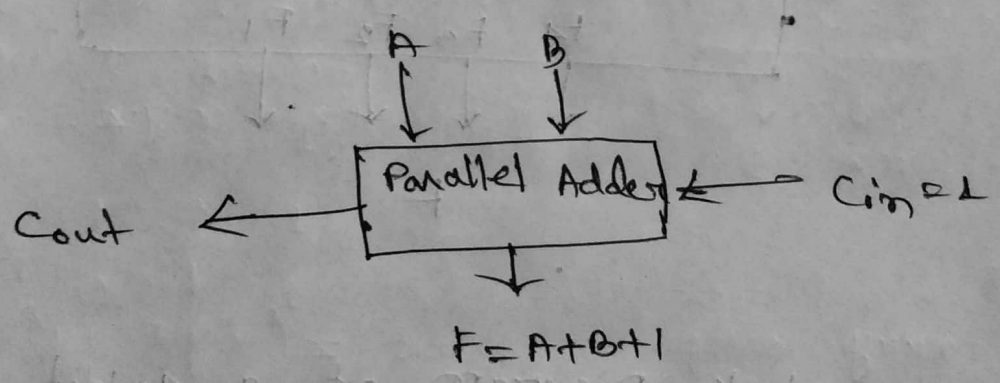

when  $s_0 = 1, s_1 = 0, cin = 1$  then  $F = A + B + 1$


⑥

iii) Transfer A

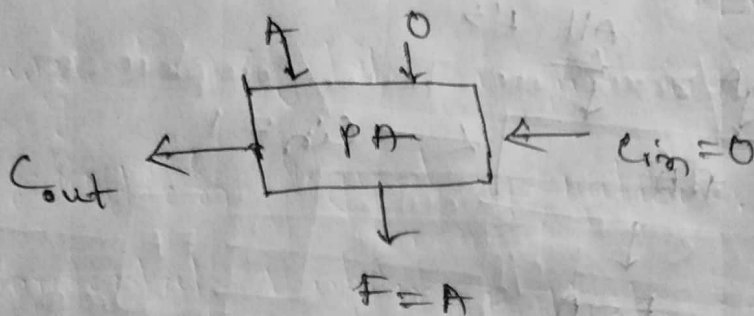


when  $S_1=0$ ,  $S_0=0$ ,  $Cin=0$  then  $F=A$

iv) Increment A

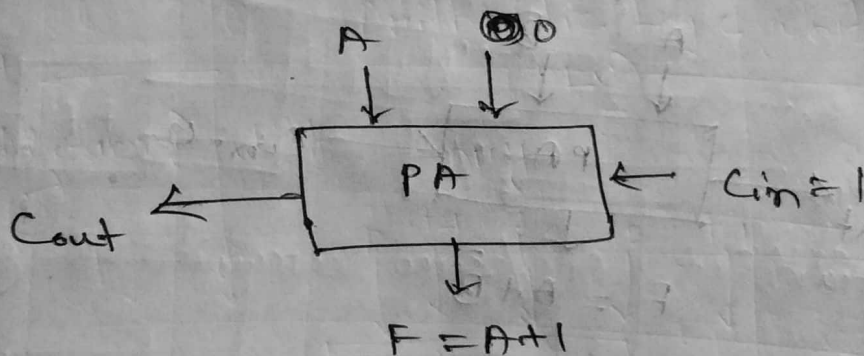

when  $S_0=0$ ,  $S_1=0$ ,  $Cin=1$  then  $F=A+1$

v) Decrement A

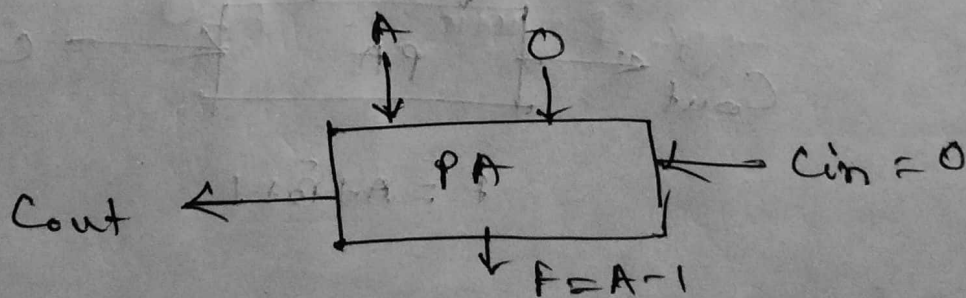


when  $S_0=1$ ,  $S_1=1$ ,  $Cin=0$  then  $F=A-1$




7

vi) Transfer A

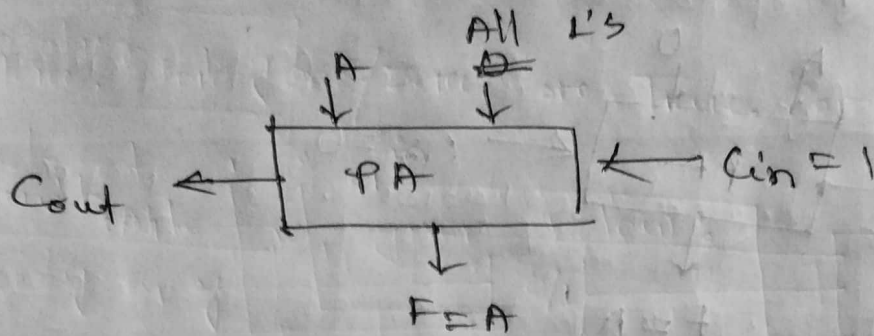


when  $s_0 = 1$ ,  $s_1 = 1$ ,  $C_{in} = 1$  then  $F = A$

vii) A plus 1's complement

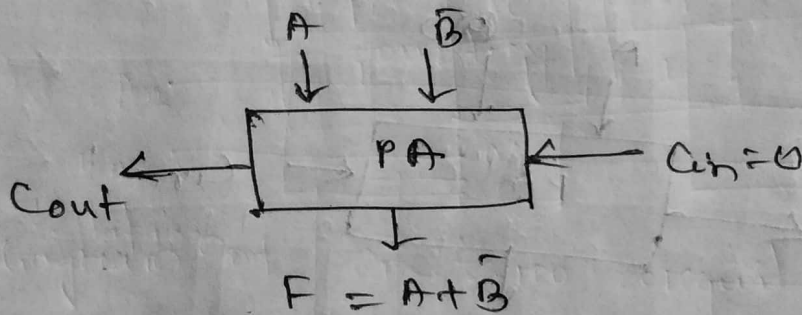

when  $s_0 = 0$ ,  $s_1 = 1$ ,  $C_{in} = 0$  then  $F = A + \bar{B}$

viii) Subtraction

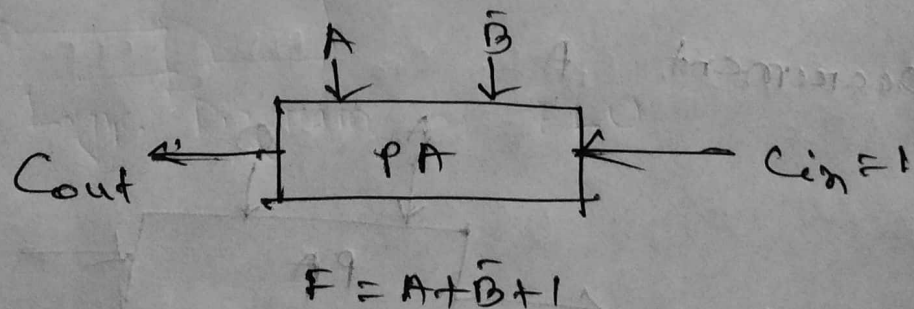


when  $s_0 = 0$ ,  $s_1 = 1$ ,  $C_{in} = 1$  then  $F = A + \bar{B} + 1$

⑧

Here, for one/zero, or True/Complement circuit, the truth table is given below:

$S_1$	$S_0$	$Y_i$
0	0	0
0	1	$B_i$
1	0	$\bar{B}_i$
1	1	1

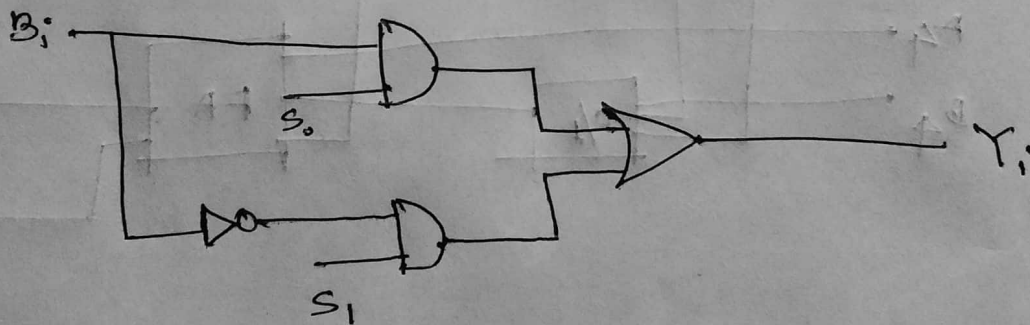
The diagram of one/zero circuit is given below:





9

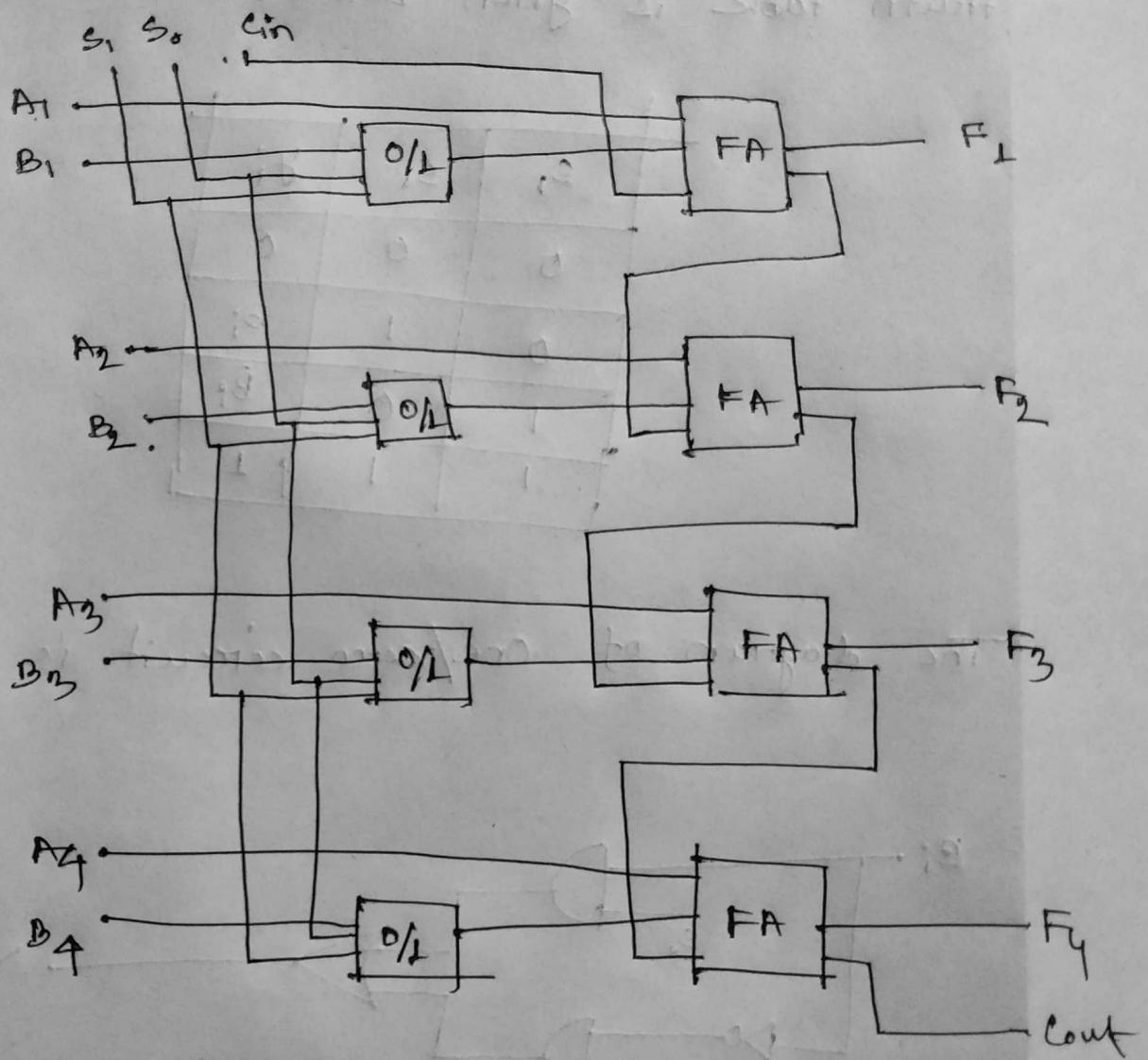The ALU diagram for 4 bits is given below:



Logic Diagram of ALU

Conclusion: In this laboratory, arithmetic circuit has been implemented using logicism. Full adder and ~~zero~~ one-zero modular circuit is included into main arithmetic circuit successfully. 8 bits arithmetic circuit is implemented and designed outputs are checked properly.